

## **IEEE's Hands on Practical Electronics (HOPE)**

### **Week 2: Voltage, Current, Resistance**

#### **Objective:**

Learn to use the Digital Multimeter (DMM)

#### **Warnings:**

Always OPEN a circuit when measuring a current. Put the DMM between the two places where you want to measure the current.

Always measure resistances after you remove the resistor from the battery.

#### **Procedure:**

1 breadboard you built last week

1 9V Battery


1 1k $\Omega$  resistor

#### **Measure:**


1) Measure the Voltage across the resistor as shown in Diagram 1

2) OPEN the circuit and measure the current as shown in Diagram 2


3) REMOVE batteries from the circuit and measure the resistance as shown in Diagram 3

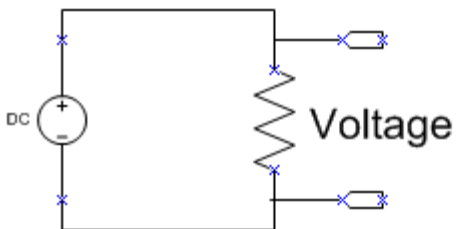

*Diagram 1*

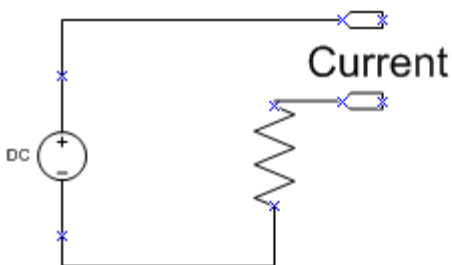


*Diagram 2*

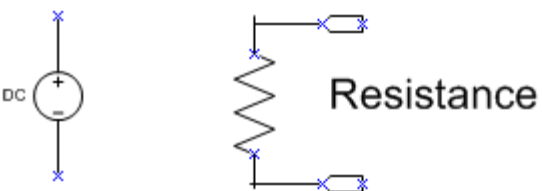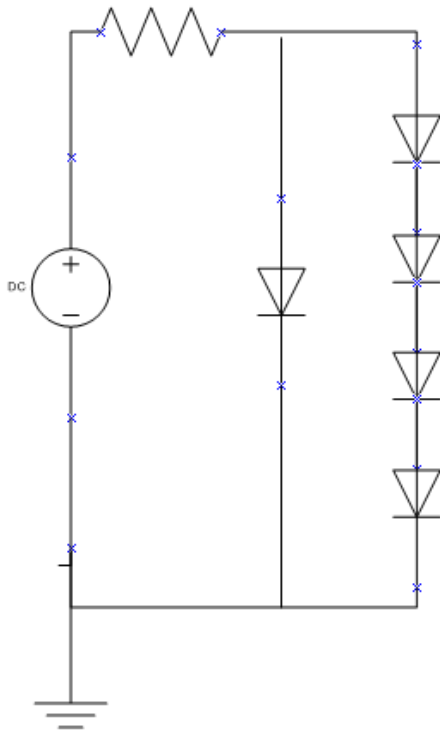

*Diagram 3*

**Part 2:**

Use your board from last week and make the following circuit.

**Questions:**

Measure the voltage across the 4 LEDs and the single LED and record their values:

How do these two measurements compare?

What did you notice about the brightness of the LEDs?

- The 4 LED's in a row
  - The 1 LED not in the row of 4
- The difference between the 4 LED's in a row and the 1 not in that row.