

## IEEE's Hands on Practical Electronics (HOPE)

### Week 9: CMOS, Digital Logic

#### Definitions:

CMOS: Complementary MOS. Uses both PMOS and NMOS in the same circuit.

Boolean Algebra: Developed by George Boole (1815-1864)

Logic: The study of the principles and criteria of valid inference

Gates: Examples: AND, OR, NOT, NAND, NOR

NAND: equivalent to an AND followed by a NOT


NOR: equivalent to an OR followed by a NOT

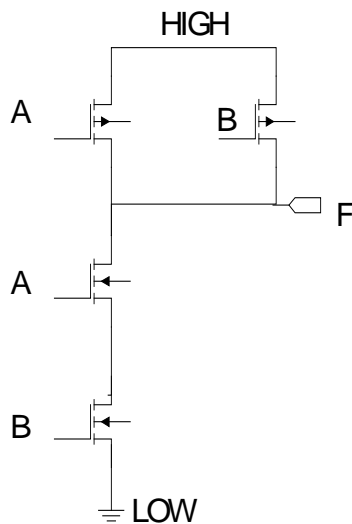
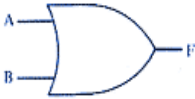
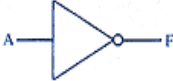


#### Conventions:

Yes or true are defined to be 1 or HIGH

No or false are defined to be 0 or LOW

Actual implementation of a NAND with transistors:



Name	Graphic Symbol	Algebraic Function	Truth Table															
AND		$F = A \cdot B$ or $F = AB$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = A + B$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT		$F = \bar{A}$ or $F = A'$	<table><tr><th>A</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
NAND		$F = (\overline{AB})$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
A	B	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = \overline{(A + B)}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	0	1	0	0	1	1	0
A	B	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

The top two transistors in parallel are PMOS, and the bottom two are NMOS.