

IEEE's Hands on Practical Electronics (HOPE)

Week 9: CMOS, Intro to Digital Logic

Objective:

Learn how CMOS technology works by analyzing how a simple CMOS NOT gate behaves.

Hints/Tips:

The transistors only have three leads that are not connected to anything.

Remember to tie the drains together somehow either with a wire or directly insert it into the same column on the breadboard.

Materials:

1 breadboard

1 9V battery


1 pMOS transistor

1 nMOS transistor

2 1.1k Ω resistors

1 LED

as many wires as necessary

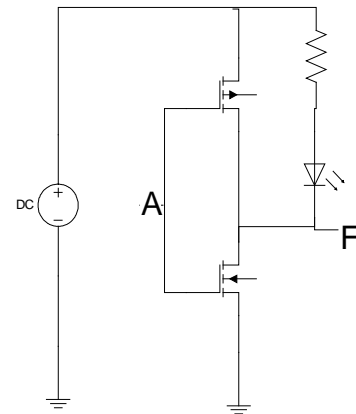


Directions:

Build the circuit shown on the right.

Connect A to V_{HIGH} and V_{LOW} and measure the voltage at F.

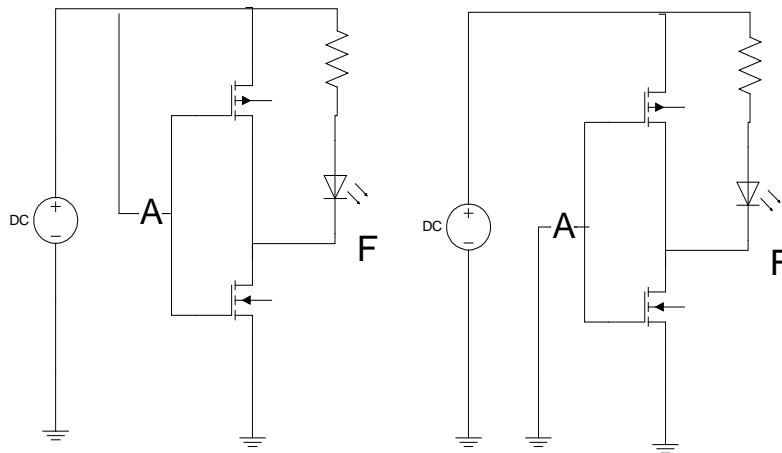The LED should turn on when the input is HIGH, and be off when the input is LOW.



Questions:

1. What is the gate symbol of the circuit above?
2. Draw two cascaded NOT gates.
3. Build a cascaded not circuit and see if it works.